


UNIT-5

FILTERS


Ryde

- Image Impedance
- Reflection Impedance of T, π , L Sections (1)
- Characteristic Impedance
- Transfer constants
- Filter fundamentals
- Design of LP, HP and BP Filters using constant-k, m-derived and composite filters (1)

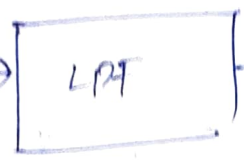$V_i = 2V$
 $f = 950Hz$
 $f = 1100$
 $\frac{V_o}{V_i} = \text{gain}$



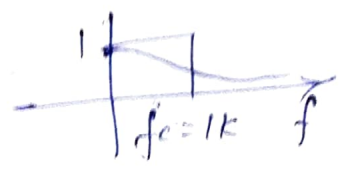$V_o = 2V, 950$
 $V_o = 0$
 $V_o = 0.2, 1100$




Passive passive

Active

Real Domain/
Time Domain


(R, L, C)

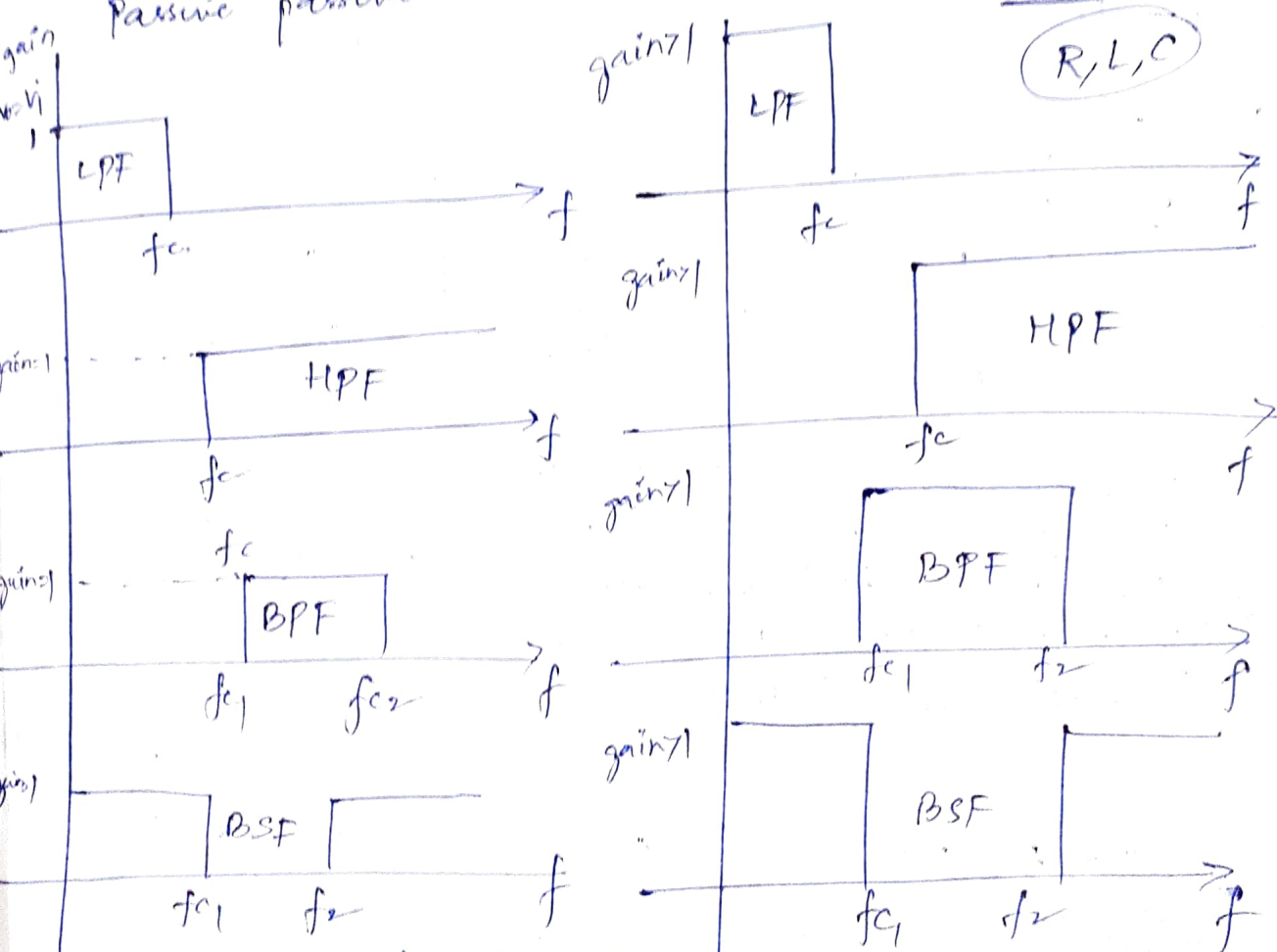

Frequency Domain :- Theoretical.

Time :- Practically possible.



Bandwidth
 $= f_{c2} - f_{c1}$

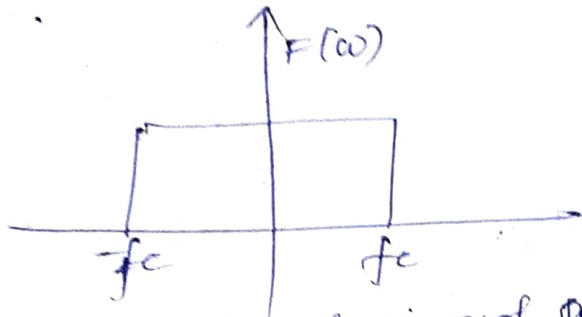



In Frequency, Bandwidth is Δf_c . Only +ve frequencies should be taken as bandwidth

Practically it is not possible to obtain -ve frequencies



Low Pass

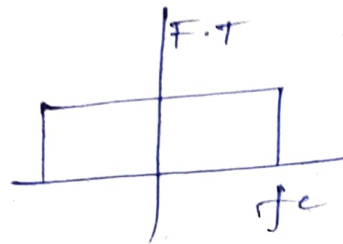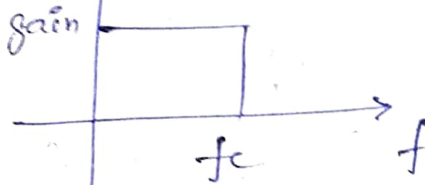

High Pass

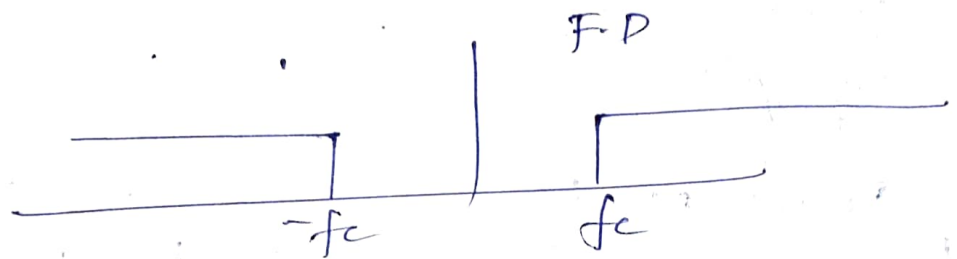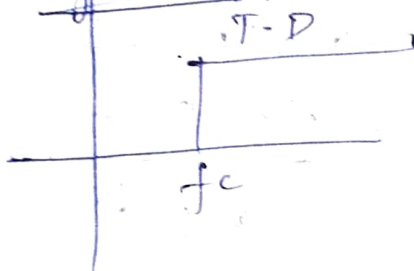


Band Pass

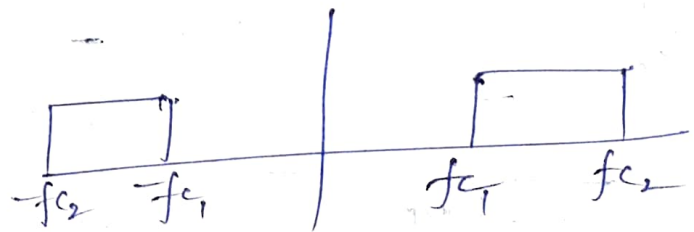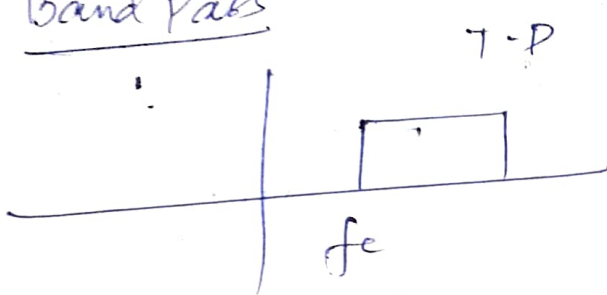



Asymmetrical N/w T, π , L

Symmetrical N/w T, π , L

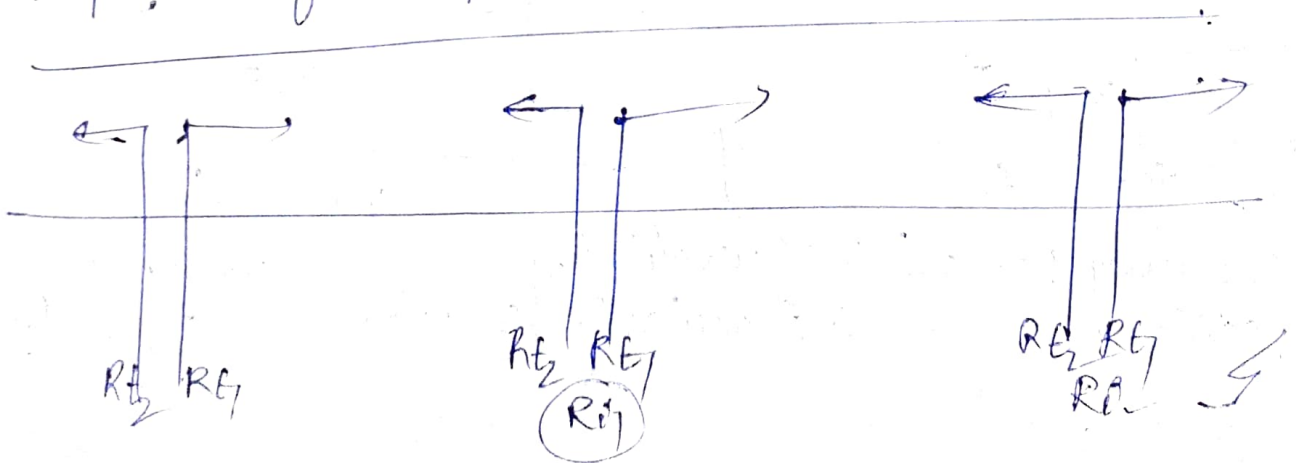Characteristic Impedance (of iterative image)
Iterative, Image Impedance.
↳ repetition of the Impedance



Assy. T. N/w: Alternative Imp.

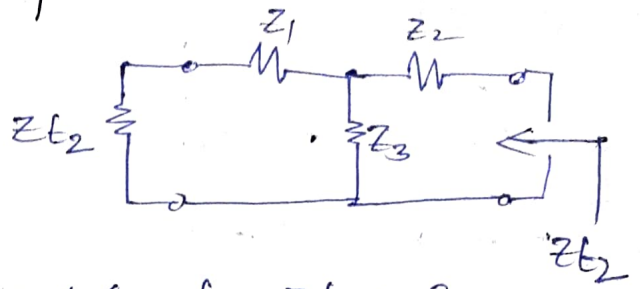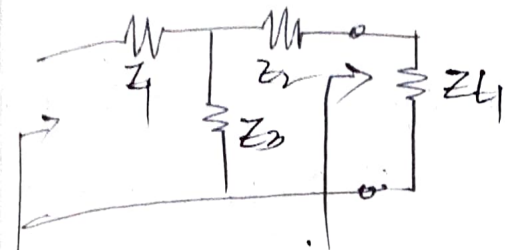


$Z_t1 = Z1 + Z3 \parallel (Z2 + Z_t1)$ — ① Solve for $Z_t1 = ?$

$$Z_t1 = \left(\frac{Z1 - Z2}{2} \right) \pm \sqrt{\left(\frac{Z1 + Z2}{4} \right)^2 + Z3(Z1 + Z2)}$$

$$Z_t2 = \left(\frac{Z2 - Z1}{2} \right) \pm \sqrt{\left(\frac{Z1 + Z2}{4} \right)^2 + Z3(Z1 + Z2)}$$


$$Z_t1 = Z_t2 = Z2 + Z3 \parallel (Z1 + Z_t2)$$

Assy. π . N/w:

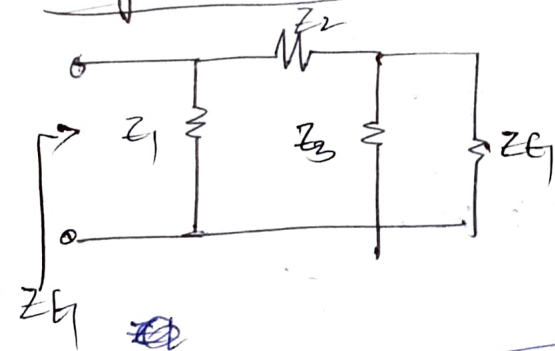

$$Z_t1 = Z1 \parallel [Z2 + (Z3 \parallel Z_t1)]$$

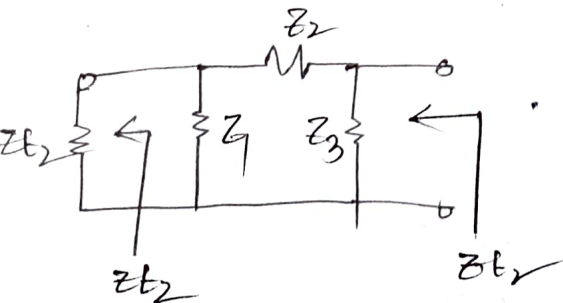
$$Z_t1 = \frac{Z1Z2 - Z2Z3 \pm \sqrt{(Z1Z2 - Z2Z3)^2 + 4Z1Z2Z3(Z1 + Z2 + Z3)}}{2(Z1 + Z2 + Z3)}$$



$$Z_t2 = Z3 \parallel [Z2 + (Z1 \parallel Z_t2)]$$

$$Z_t2 = \frac{(Z2Z3 - Z1Z2) \pm \sqrt{(Z1Z2 - Z2Z3)^2 + 4Z1Z2Z3(Z1 + Z2 + Z3)}}{2(Z1 + Z2 + Z3)}$$

Image Imp/! to Asy. T N/w

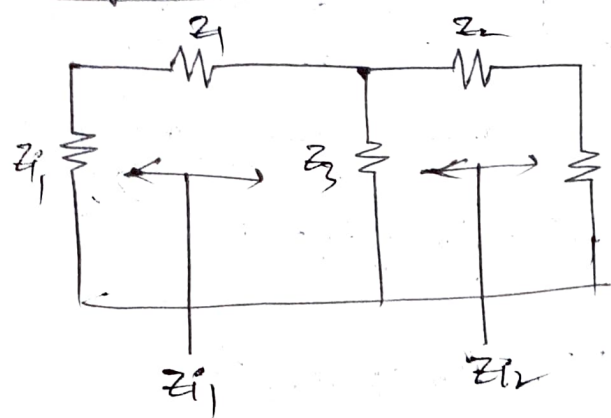


$$Z_{i1} = Z_1 + [Z_3 \parallel (Z_2 + Z_{i2})] \quad \text{--- (1)}$$

$$Z_{i2} = Z_2 + [Z_3 \parallel (Z_1 + Z_{i1})] \quad \text{--- (2)}$$

Solve for $Z_{i1} = \sqrt{(Z_1 + Z_3)(Z_1 + Z_2 \parallel Z_3)}$

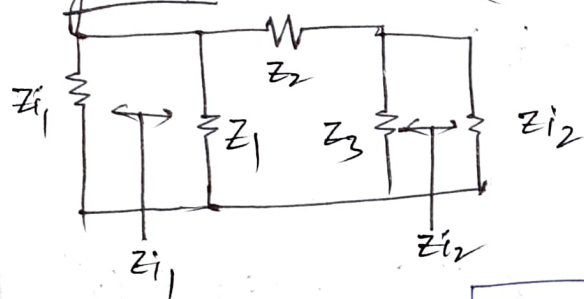Asy. T N/w. $Z_{i2} = \sqrt{(Z_2 + Z_3)(Z_2 + Z_1 \parallel Z_3)}$




$$Z_{i1} = Z_1 \parallel [Z_2 + (Z_3 \parallel Z_{i2})] \quad \text{--- (1)}$$

$$Z_{i2} = Z_3 \parallel [Z_2 + (Z_1 \parallel Z_{i1})] \quad \text{--- (2)}$$

Solve for $Z_{i1} = \sqrt{Z_1 \parallel (Z_2 + Z_3)(Z_1 \parallel Z_2)}$

$$Z_{i2} = \sqrt{Z_3 \parallel (Z_2 + Z_1)(Z_2 \parallel Z_3)}$$

Image transfer const = O_i

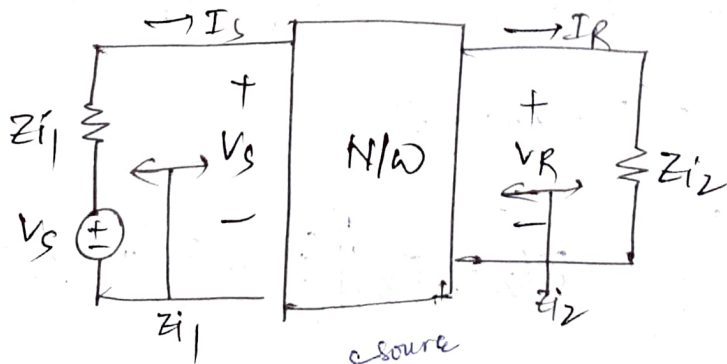

$$O_i = \frac{1}{2} \log_e \left(\frac{V_S I_S}{V_R I_R} \right) = \frac{1}{2} \log_e \frac{Z_{i1} \cdot I_S^2}{Z_{i2} \cdot I_R^2}$$

$$= \log_e \sqrt{\frac{Z_{i1}}{Z_{i2}} \cdot \frac{I_S}{I_R}}$$

For symmetrical Network $Z_{i1} = Z_{i2}$

$$0_i = \log_e \frac{I_s}{I_R}$$

$$N = e^{0_i} = \frac{I_s}{I_R} = e^{\gamma} = e^{(\alpha + j\beta)}$$


$$\ln N = \ln \left(\frac{I_s}{I_R} \right) = \alpha$$

γ = propagation constant
 α = Attenuation constant
 in Nepers.

$$\begin{aligned} \text{Attenuation in dB} &= 10 \log_{10} \frac{P_s}{P_R} \\ &= 20 \log_{10} \frac{I_s}{I_R} \\ &= 2 \log_{10} e \log_e \frac{I_s}{I_R} \end{aligned}$$

$$\boxed{\text{Attenuation in dB} = 8.686 [\text{Attenuation in Nepers}]}$$

Propagation const. for sym /: T. No

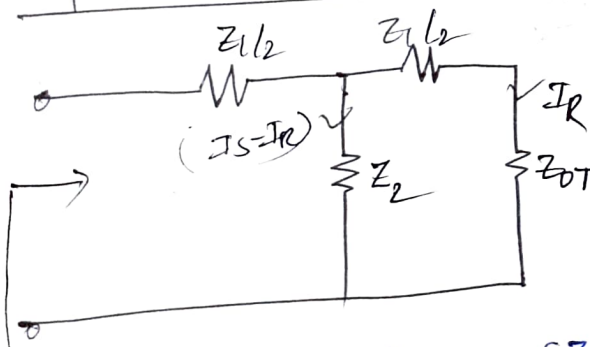


$$Z_{0T} + Z_2(I_s - I_R) = I_R \left(\frac{Z_1}{2} + Z_0 \right)$$

$$Z_2 I_s = I_R \left[\frac{Z_1}{2} + Z_0 + Z_2 \right]$$

$$\frac{I_s}{I_R} = e^{\gamma} = \frac{\frac{Z_1}{2} + Z_0 + Z_2}{Z_2}$$

$$Z_0 = Z_2 (e^{\gamma} - 1) - \frac{Z_1}{2}$$
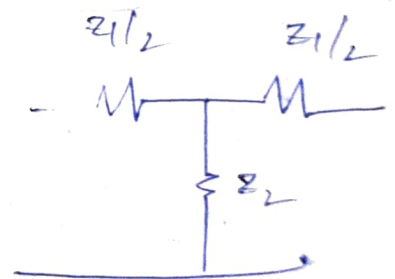
$$\sqrt{\frac{Z_1^2}{4} + Z_1 Z_2} = Z_2 (e^{\gamma} - 1) - \frac{Z_1}{2}$$



$$Z_{01} = Z_{02} = Z_{i1} = Z_{i2} = Z_0$$

$$Z_{0\pi} = \sqrt{\frac{Z_1 Z_2}{1 + Z_1/4 Z_2}}$$

$$\begin{aligned} Z_{0T} &= \sqrt{\left(\frac{Z_1}{2} + Z_2 \right) \left(\frac{Z_1}{2} + \left(\frac{Z_1 Z_2}{2} \right) \right)} \\ &= \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4 Z_2} \right)} \\ &= \sqrt{Z_1 Z_2 + \frac{Z_1^2}{4}} \end{aligned}$$

$$\frac{z_1^2}{4} + z_1 z_2 = z_2^2 (e^{2\gamma} + 1 - 2e^\gamma) + \frac{z_1^2}{4} - z_1 z_2 (e^\gamma - 1)$$

$$\frac{e^{2\gamma} + 1 - 2e^\gamma}{e^\gamma} = \frac{z_1}{z_2}$$

$$e^\gamma + e^{-\gamma} - 2 = \frac{z_1}{z_2}$$

$$\frac{e^\gamma + e^{-\gamma}}{2} = 1 + \frac{z_1}{2z_2}$$

$$\cosh \gamma = 1 + \frac{z_1}{2z_2}$$

$$\sinh \frac{\gamma}{2} = \sqrt{\frac{1}{2} [\cosh \gamma - 1]}$$

$$\boxed{\sinh \frac{\gamma}{2} = \sqrt{\frac{z_1}{4z_2}}} \\ \div \sinh \frac{\gamma}{2}$$

06/11/2019

FILTER FUNDAMENTALS

$$\sinh \frac{\gamma}{2} = \sqrt{\frac{z_1}{4z_2}}$$

$$\sinh \left(\alpha + j\beta \right) = \sinh \frac{\alpha}{2} \cos \frac{\beta}{2} + j \cosh \frac{\alpha}{2} \sin \frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}}$$

1) If z_1 & z_2 are same type of element; $\frac{z_1}{4z_2} > 0$;

$$\sqrt{\frac{z_1}{4z_2}} \text{ is real.}$$

$$\sqrt{\frac{z_1}{4z_2}} \text{ is real.}$$

$$\cosh \frac{\alpha}{2} \sin \beta = 0$$

$$\sin \beta/2 = 0$$

$$\sinh \frac{\alpha}{2} \cos \frac{\beta}{2} = \sqrt{\frac{z_1}{4z_2}}$$

$$\cos \beta/2 = 1$$

if $\frac{\beta}{2} = n\pi$, $n=0,1,2,\dots$

$$\alpha = 2 \sinh^{-1} \sqrt{\frac{Z_1}{4Z_2}}$$

II) If Z_1 & Z_2 opposite type of elements

$$\sinh \frac{\alpha}{2} \cos \frac{\beta}{2} = 0$$

$$\cosh \frac{\alpha}{2} \sin \frac{\beta}{2} = \sqrt{\frac{Z_1}{4Z_2}}$$

a) $\sinh \frac{\alpha}{2} = 0$

$$\alpha = 0$$

$$\beta = 2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}}$$


b) $\cos \frac{\beta}{2} = 0$ $\sin \frac{\beta}{2} = \pm 1$

$$\beta = (2n+1)\pi$$

$$\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}}$$

$\frac{Z_1}{4Z_2}$	$+\infty$ to 0	0 to -1	-1 to $-\infty$
Reactance type	same	opp	oppo
Band	stop	pass	stop
α	$2 \sinh^{-1} \sqrt{\frac{Z_1}{4Z_2}}$	0	$2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}}$
β	π	$2 \sin^{-1} \sqrt{\frac{Z_1}{4Z_2}}$	π

Const K-LPF:

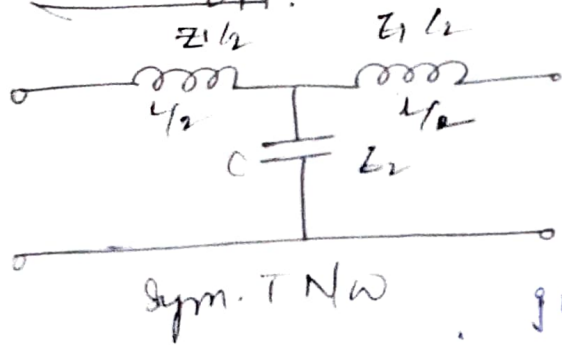


$$Z_1 = j\omega \left(\frac{L}{2}\right)$$

$$\frac{Z_1}{4Z_2} = -1$$

$$Z_1 = -4Z_2$$
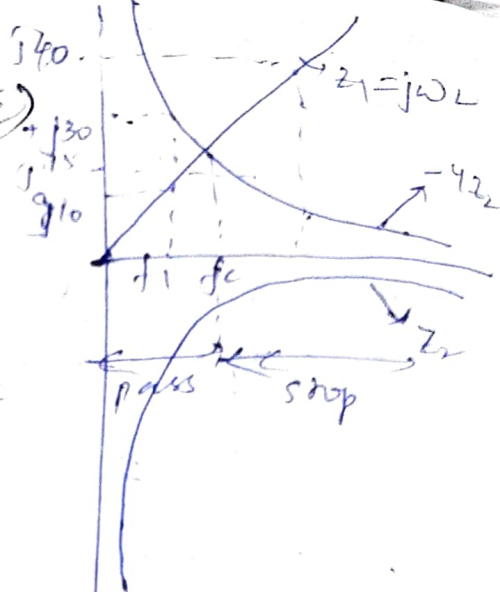
$$j\omega_c L = -4 \times \frac{1}{j\omega_c C}$$



$$\text{at } f_1 \quad \frac{Z_1}{4Z_2} = \frac{j10}{-j30} = -\frac{1}{3} \quad (0 \text{ to } -1)$$

$$\text{at } f_2 \quad \frac{Z_1}{4Z_2} = \frac{j40}{-j15} = -3 \quad (-1 \text{ to } -\infty)$$

$$4Z_1 = j\omega L \times \frac{1}{j\omega C} = \frac{L}{C} = R_k^2 \quad \boxed{R_k = \sqrt{\frac{L}{C}}} \quad (1)$$

$$R_L = R_0 = R_k = \sqrt{\frac{L}{C}}$$

$$\frac{Z_1}{4Z_2} = -1$$

$$Z_1 = -4Z_2$$

$$j\omega_c L = -4 \times \frac{1}{j\omega_c C}$$

$$j/2\pi f_c L = -\frac{4}{j2\pi f_c C}$$

$$R_k = j\omega_c L$$

$$\boxed{f_c = \frac{1}{\pi \sqrt{LC}}}$$

Ans-3

Q) Design a constant K .t and π type Low pass filter for the following specification Given f_c = cut off frequency $R_0 = 60 \Omega$

$$\frac{L}{C} = 600, \quad \frac{1}{\pi \sqrt{LC}} = 2 \times 10^3$$




$$\frac{1}{\pi C} = 2 \times 10^3 \Rightarrow C = \frac{1}{2\pi \times 10^3} = 1.59 \times 10^{-4} F = 159 \mu F$$

$$\sqrt{\frac{L}{C}} = 600$$


$$\frac{L}{C} = 600 \times 600$$

$$L = 600 \times 600 \times 159 \times 10^6$$

$$L = 57.29 \text{ H}$$

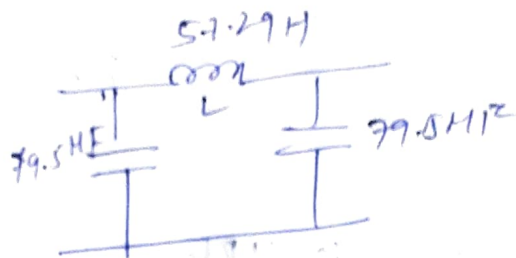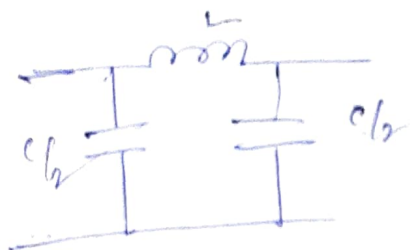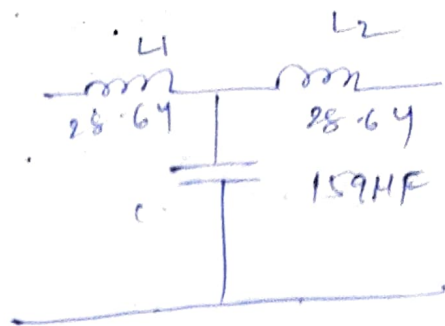

Const-k - LPT

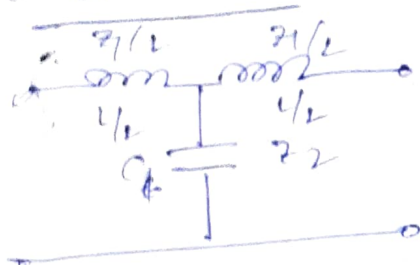


T-type

$$Z_1 Z_2 = \frac{L}{C} = Rk^2$$

$$Rk = \sqrt{\frac{L}{C}} \quad (1)$$

$$Z_1 = -4Z_2$$
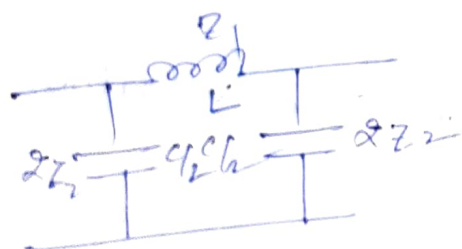
$$\alpha = 2 \cosh^{-1} \sqrt{\frac{Z_1}{4Z_2}} = 2 \cosh^{-1} \left(\frac{f}{f_c} \right)$$



$$f_c = \frac{1}{\pi \sqrt{LC}} \quad (2)$$

$$\frac{L}{C} = \pi^2 LC = \frac{1}{f_c^2}$$

$$\frac{Z_1}{4Z_2} = \frac{j\omega L}{4 \times -\frac{j}{\omega C}} = -\frac{\omega^2 LC}{4}$$

$$= -\frac{(2\pi f)(2\pi f)LC}{4}$$

$$= -\frac{f^2}{f_c^2} = -\left(\frac{f}{f_c}\right)^2$$

$$\boxed{B = 2 \sin^{-1} \left(\frac{f}{f_c} \right)}$$

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2}\right)}$$

$$= \sqrt{R_k^2 \left(1 - \left(\frac{f}{f_c}\right)^2\right)^2}$$

$$\frac{Z_{OT}}{R_k} = \sqrt{1 - \left(\frac{f}{f_c}\right)^2}$$

Ass-3
Q

⑥ Design constant-K HPF [T & B] for following specifications

a) $f_c = 2k$

$R_o = 600\Omega$

b) draw α, β ; NOT
(Normalised characteristic impedance)

c) find α at 1KHz

β at 3.5KHz

Z_{OT} at 1.5K & 3K


Ass-3

⑦ Draw the α, β, Z_{OT} characteristic impedance variations in both the bands. (pass & stop)



e) Find the value of α at $f = 3K$

d) What is the value of phase constant at $f = 1.5K$


e) Calculate β at $f = 1.5K$

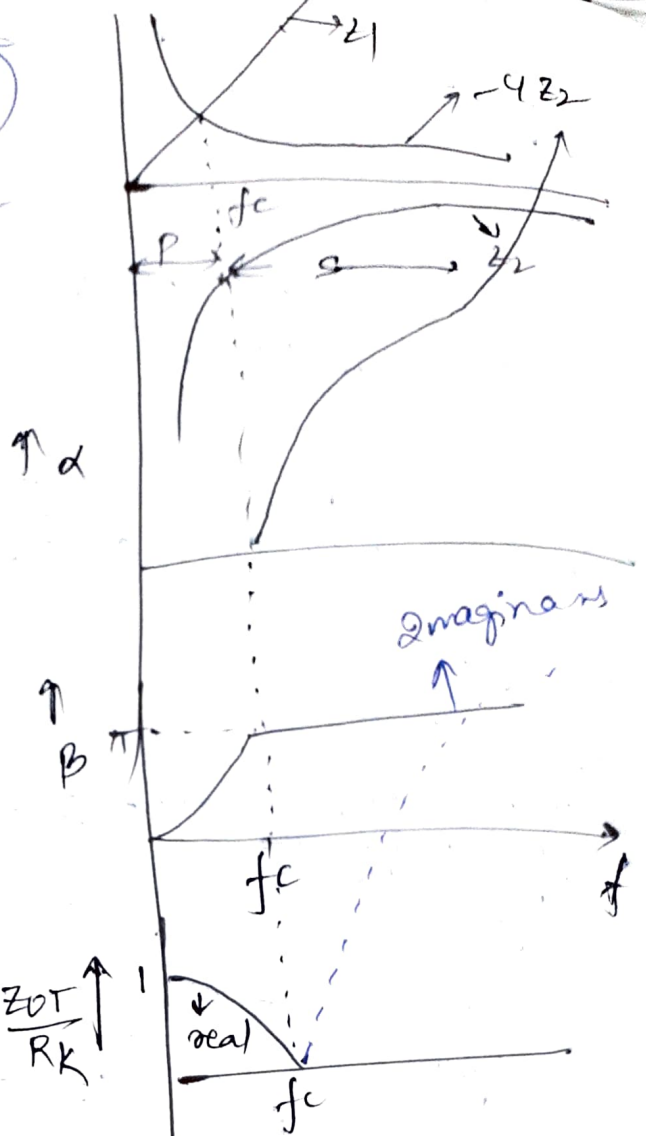

Const - k - HPP

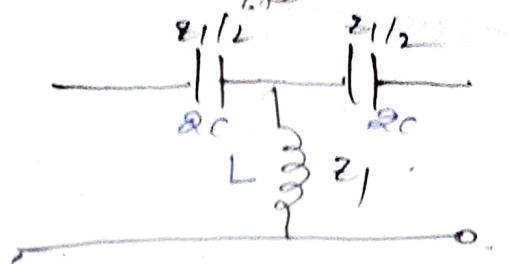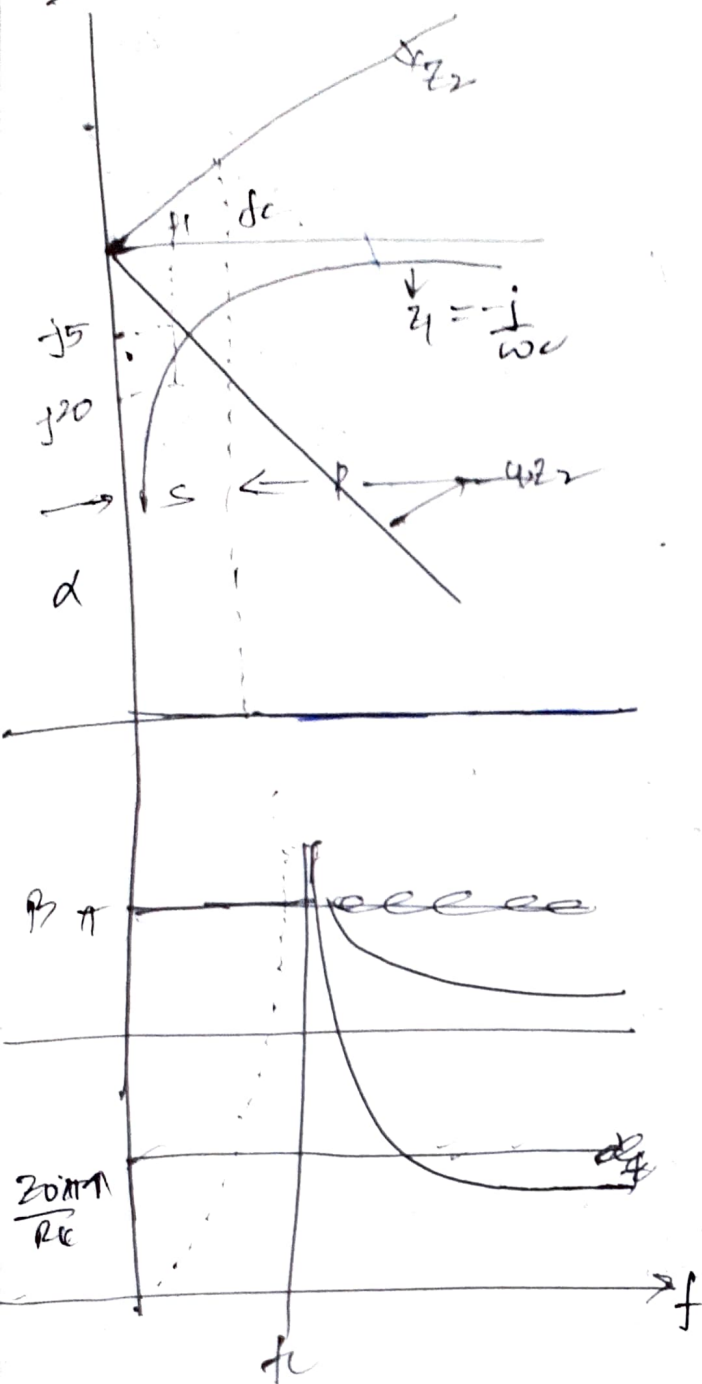
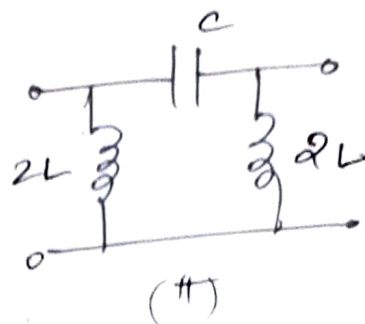
$$z_1/2 = \frac{-j}{\omega c/2} = \frac{j}{\omega c}$$



$$z_1 = -4z_2$$

$$\frac{z_1}{4z_2} = 0 \text{ to } -1 \text{ pass.}$$

$$-1 \text{ to } -\infty \text{ stop}$$

$$\frac{z_1}{4z_2} = \frac{-j20}{j5} = -4$$

$$z_1 z_2 = \frac{L}{C} = R_k^2$$

$$R_k = \sqrt{\frac{L}{C}} \quad (1)$$

$$z_1 = -4z_2$$

$$\frac{-j}{\omega c} = -4 \times j\omega L$$

$$d = 2 \cosh^{-1} \sqrt{\frac{z_1}{4z_2}} = \frac{-j}{\omega c} \frac{1}{4 \times j\omega L}$$

$$= \frac{-1}{8\omega^2 LC}$$

$$= -1$$

$$8 \times 20 \times 1 \times 2 \times 10^{-9} \times 10^{-6} \times 10^6$$

$$4\omega^2 LC = 1 \quad f_c = \frac{1}{4\pi\sqrt{LC}} \quad (2)$$

$$\omega^2 = \frac{1}{4LC}$$

$$\omega = \frac{1}{2\sqrt{LC}} \quad f_c = \frac{1}{4\pi\sqrt{LC}}$$

$$\sqrt{LC} = \frac{1}{4\pi f_c}$$

$$d = 2 \cosh^{-1} \sqrt{\frac{Z_1}{f Z_2}}$$

$$LC = \frac{1}{\omega^2 LC}$$


$$\begin{aligned} \frac{Z_1}{f Z_2} &= \frac{\frac{-j}{\omega C}}{4j\omega L} = \frac{-j}{4\omega^2 LC} = \frac{-j \times 16\pi^2 f^2 LC}{4\omega^2} \\ &= \frac{-2 \times \pi^2 f^2 LC}{2\pi f \times 2\pi f} \\ &= -\frac{f^2 C^2}{f^2} \end{aligned}$$

$$\begin{aligned} 2 \cosh^{-1} \left(\sqrt{\frac{Z_1}{f Z_2}} \right) &= 2 \cosh^{-1} \left(\sqrt{\frac{-f C^2}{f^2}} \right) \\ &= 2 \cosh^{-1} \left(\frac{f C}{f} \right) \end{aligned}$$

$$\frac{Z_{OT}}{R_0} = \sqrt{1 - \left(\frac{f C}{f} \right)^2}$$

$$Z_{OT} = \sqrt{\frac{Z_1 Z_2}{1 + \frac{Z_1}{4Z_2}}}$$

const- ϵ -BPF:

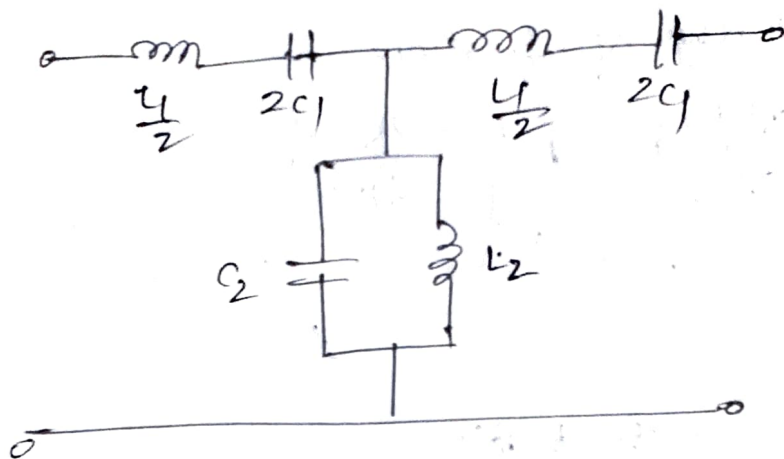

$$f_s = f_p$$

$$\omega_{os} = \frac{1}{\sqrt{L_1 C_1}}$$

$$\omega_{op} = \frac{1}{\sqrt{L_2 C_2}}$$

$$\textcircled{1} \quad L_1 C_1 = L_2 C_2$$

$$\textcircled{2} \quad Z_1 Z_2 = \left(j\omega L_1 - \frac{j}{\omega C_1} \right) \left(j\omega L_2 + \frac{j}{\omega C_2} \right)$$

$$\boxed{\frac{L_2}{C_1} = \frac{L_1}{C_2} = R_k^2}$$



$$\textcircled{3} \quad f_0 = \sqrt{f_1 f_2}$$

$$Z_1 = -4 Z_2$$

$$Z_1^2 = -4 R_k^2$$

$$Z_1 = \pm j 2 R_k$$
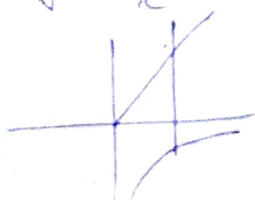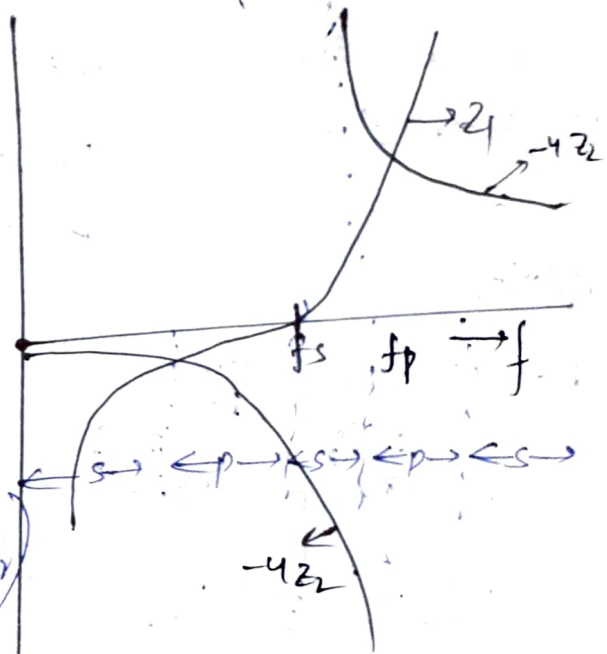
$$j\omega L_1 - \frac{j}{\omega C_1} = j 2 R_k$$



Q) Design a constant k band pass filter, T and π type
 (1) for the following specifications

(i) Lower cut off frequency, $f_{c1} = 2K \text{ Hz}$

(ii) Higher cut off frequency, $f_{c2} = 4K \text{ Hz}$


(iii) Characteristic resistance ($R_0 = R_k = 500\Omega$)

Theory
Disadvantage of constant- k :

- (1) Attenuation constant varying slowly in stop band.
- (2) Characteristic impedance is varying in pass band
 - due to which impedance matching not done

13/11/2019

M-derived T-type

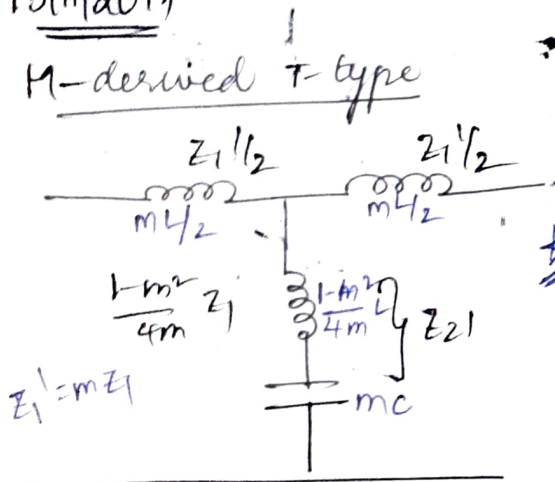

at f_∞

$$\left| \frac{1-m^2}{4m} Z_1 \right| = \left| \frac{Z_2}{m} \right|$$

$$f_\infty = \frac{f_c}{\sqrt{1-m^2}} \text{ for LPF}$$

$$f_\infty = f_c \sqrt{1-m^2} \text{ for HPF}$$



$$Z_1 = j2\pi f L$$

$$Z_2 = \frac{1}{j2\pi f C}$$

$$f_c = \frac{1}{\pi \sqrt{LC}}$$

$$Z_{OT} = \sqrt{Z_1 Z_2 \left(1 + \frac{Z_1}{4Z_2} \right)} = \sqrt{m Z_1 Z_2' \left(\frac{1+mZ_1}{4Z_2} \right)}$$
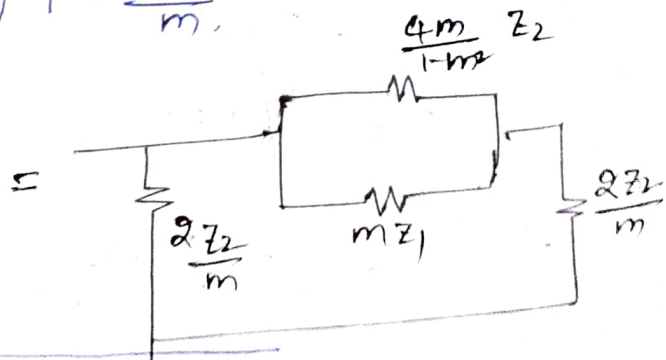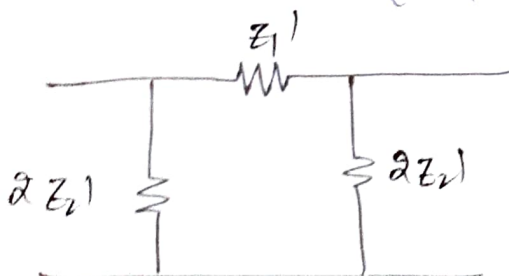
$$\text{Solve for } Z_2' = \left(\frac{1-m^2}{4m} \right) Z_1 + \frac{Z_2}{m}$$



$$Z_{OT} = \sqrt{\frac{Z_1 Z_2}{1 + Z_1/4Z_2}} = \sqrt{\frac{Z_1' Z_2/m}{1 + \frac{Z_1'}{4Z_2/m}}}$$

Solve for $Z_1' = \frac{1}{\frac{1}{mZ_1} + \frac{1}{\left(\frac{4m}{1-m^2}\right)Z_2}}$

$\textcircled{1} f_c = \frac{1}{\pi \sqrt{LC}}$
 $\textcircled{2} R_o = \sqrt{\frac{L}{C}}$
 $\textcircled{3} f_{\infty} = \frac{f_c}{\sqrt{1-m^2}}$

how to design
design m-derived T-type.

Theory of

Disadvantage of m-derived:

(i) Characteristic impedance is still changing in m-derived. In pass band.
It can be eliminated by taking $m=0.6$ and bisection

Q) Design a composite LPF + -type filter with the following specification.

(i) $f_c = 2K$, (ii) $R_o = 600\Omega$, (iii) $f_{\infty} = 2.2K$

$$f_c = \frac{1}{\pi \sqrt{LC}} = 2 \times 10^3$$

$$R_o = \sqrt{\frac{L}{C}} = 600$$

$$\sqrt{\frac{L}{C}} = 600$$

$$\frac{L}{C} = 36 \times 10^4$$

$$\frac{L}{C} = 36 \times 10^4$$

$$L = 0.26 \times 10^{-6} \times 36 \times 10^4 = 9.36 \times 10^{-2}$$

$$L = 93.6 \times 10^{-3} = 93.6 \text{ mF}$$

$$f_{\infty} = \frac{f_c}{\sqrt{1-m^2}}$$

$$2.2 \times 10^3 = \frac{2 \times 10^3}{\sqrt{1-m^2}}$$

$$\sqrt{1-m^2} = \frac{1}{1.1}$$



$$\sqrt{1-m^2} = 0.8264$$

$$m^2 = \frac{21}{121} = \frac{\sqrt{21}}{11} = 0.416$$


Composite LPF + -type

" π
HPF T
" π

Constant LPF - T/ π
HPF - T/ π
BP - T/ π

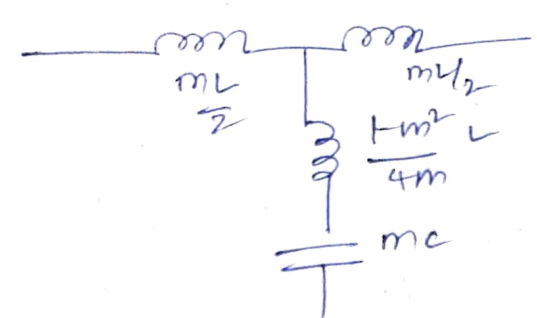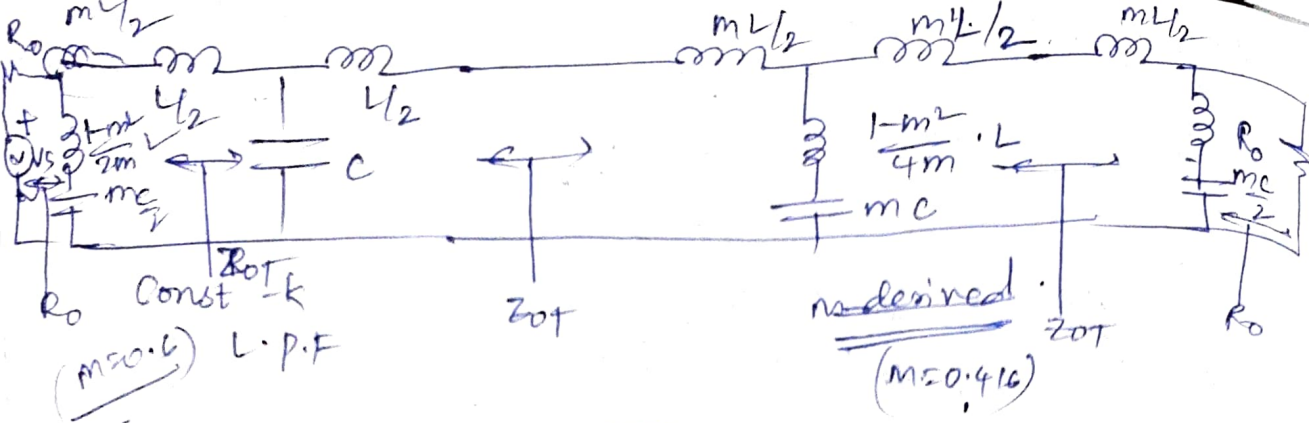

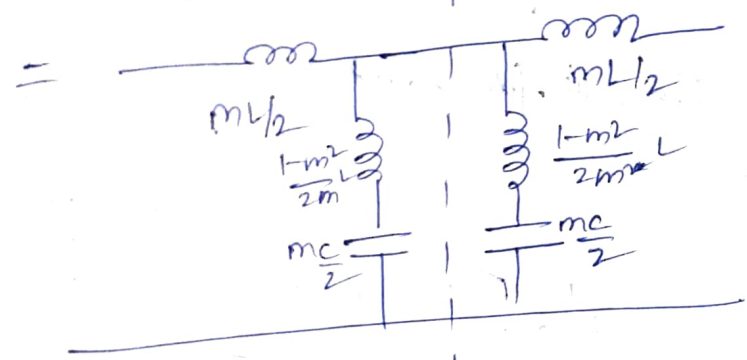With $m=0.6$ \rightarrow compulsion \rightarrow Characteristic impedance will match.



$$\frac{\frac{L}{2} \times \frac{L}{2}}{L} = \frac{L}{4}$$

