


08th August 2019

UNIT 2: TRANSIENT ANALYSIS.

- RC

- RL

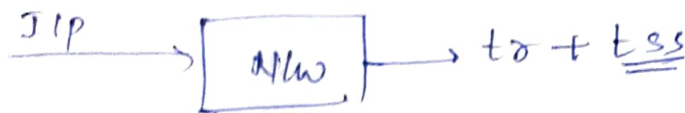
- RLC series and parallel circuits with DC
- Step, impulse, ramp, exponential and AC response using
Time Domain and Laplace transform methods.



Even if current is sent suddenly, it will behave peculiarly.

1st order - short cut, 1st & 2nd → Mathematical, 3rd & above - Laplace. any order.

RC TRANSIENT:

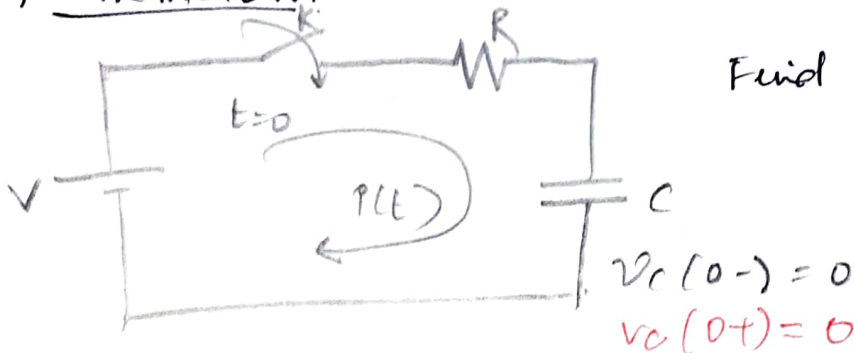

Find $i(t)$ for $t > 0$ (0^+ to ∞)

$$v = Ri(t) + \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$v_C(t) = \frac{1}{C} \int_{-\infty}^t i(t) dt$$

$$v_C(0^+) = \frac{1}{C} \int_{-\infty}^{0^-} i(t) dt + \frac{1}{C} \int_{0^-}^{0^+} i(t) dt + \frac{1}{C} \int_{0^+}^t i(t) dt$$

$$= v_C(0^-) + 0$$

$$v_C(0^+) = v_C(0^-)$$

$$v = Ri(t) + \frac{1}{C} \int_{0^+}^t i(t) dt$$

$$i(0^-) = 0$$

$$i(0^+) = \frac{v}{R}$$

i changing suddenly but not v
ie why. we have transient
nature in capacitor.

Not impulse as $R \neq 0$


$$\int_a^b f(t) dt = 0$$

If it is impulse
 $\int_a^b f(t) dt = 1$

(1) Voltage in Capacitor is a continuous function of time.

Current is a discontinuous function of time.

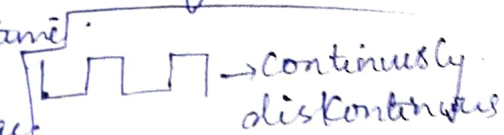(2) Capacitor opposes sudden change of voltage.
 Capacitor will not oppose sudden change of current.



→ Continuously discontinuous

$V(t) \rightarrow$ discontinuous
 $V(0^-) = 0$
 $V(0^+) = 1$
 value of discontinuity $\neq 1$

(3) Voltage is a continuous function.
 Capacitor smoothen the voltage wave, but it will not smoothen the current wave

$$\rightarrow V = Ri(t) + \frac{1}{C} \int_0^t i(t) dt$$


$$0 = R \frac{di}{dt} + \frac{i}{C}$$

$$\left(D + \frac{1}{RC}\right)i = 0 \quad \text{1st order homogeneous D.E}$$

$$i = i_c(t)$$

14th August 2019

RC TRANSIENT:

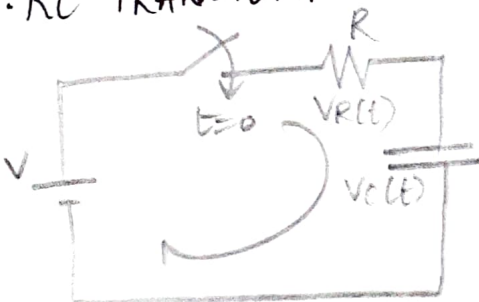

$$V = Ri(t) + \frac{1}{C} \int_0^t i(t) dt$$

$$0 = R \frac{di}{dt} + \frac{i}{C}$$

$$\left(D + \frac{1}{RC}\right)i = 0$$

$$i(t) = i_c(t) = k e^{-t/RC}$$

$$\Rightarrow V_C(0^-) = V_C(0^+) = i_C(0^-) = 0$$


$$i(0^+) = \frac{V}{R} = k \times 1 = k \Rightarrow k = \frac{V}{R}$$

Hence

$$i(t) = \frac{V}{R} e^{-t/RC} \quad \text{for } t > 0$$

$$V_R(t) = R \cdot i(t) = V e^{-t/RC}$$
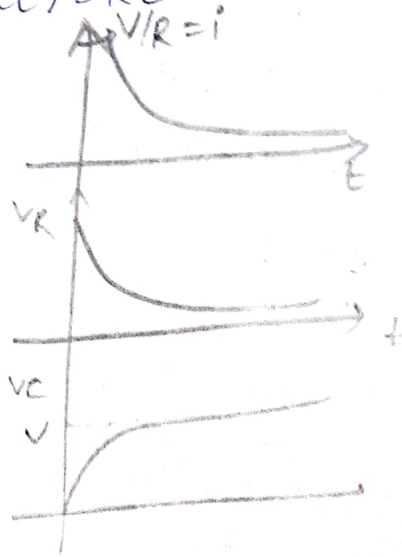
$$V_C(t) = \frac{1}{C} \int_0^t i(t) dt = \frac{1}{C} \int_0^t \frac{V}{R} e^{-t/RC} dt$$



$$V_C(t) = V(1 - e^{-\frac{t}{RC}})$$


$i(\infty) = 0 \rightarrow$ In steady state capacitor behaves as Open

Initially V_C is 0, \Rightarrow short

$$V_C(t=RC) = V[1 - e^{-1}] = 0.63V$$

$\tau \rightarrow$ time taken to reach final value

$\tau \rightarrow$ time const

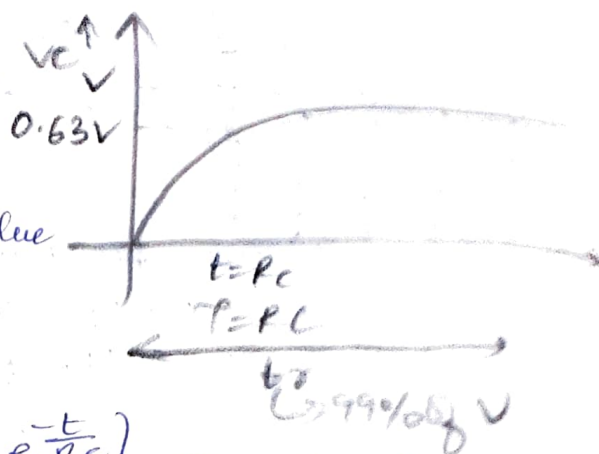


• Power in the Capacitor,

$$P_C(t) = V_C(t)i(t) = V[1 - e^{-\frac{t}{RC}}] \left[\frac{V}{R} e^{-\frac{t}{RC}} \right] \quad \text{Here } RC = \tau$$

$$P_C(t) = \frac{V^2}{R} \left[e^{-\frac{t}{\tau}} - e^{-\frac{2t}{\tau}} \right]$$

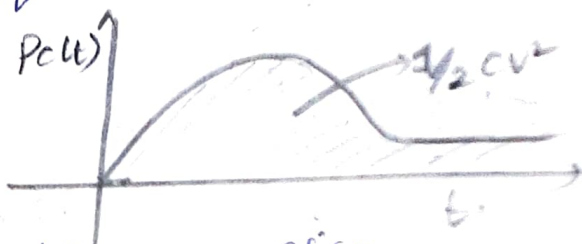
$$E_C = \int_0^{\infty} P_C(t) dt = \frac{1}{2} CV^2$$



$$P_R(t) = V_R(t) \cdot i(t) = V e^{-t/\tau} \cdot \frac{V}{R} e^{-t/\tau} = \frac{V^2}{R} e^{-2t/\tau}$$

$$E_R(t) = \int_0^{\infty} P_R(t) dt = \frac{1}{2} CV^2$$
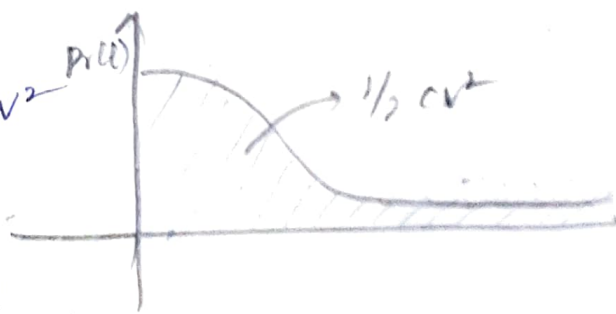
$$V = V_R + V_C = \frac{1}{2} CV^2 + \frac{1}{2} CV^2 = CV^2$$



Efficiency, $\eta = \frac{\text{Energy stored}}{\text{Energy supplied}}$


$$= \frac{\frac{1}{2} CV^2}{CV^2} = 50\%$$

$\eta \rightarrow$ independent of R & C

$\rightarrow \tau = RC$ If $R \downarrow$ & $C \downarrow \Rightarrow \tau \downarrow$

If transient time (τ) less, Capacitor charges slowly

Dual of RC:

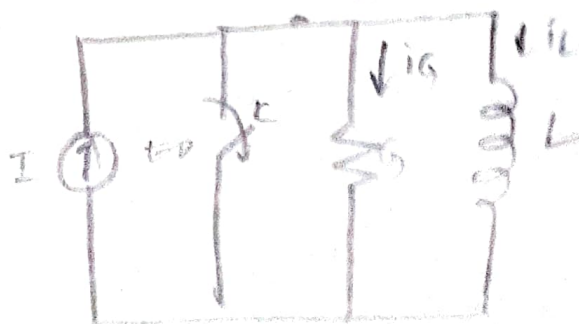

$$I = G v(t) + \frac{1}{L} \int_0^t v(t) dt$$

$$0 = G v(t) + \frac{1}{L} \int_0^t v(t) dt$$

21st August 2019

(Continuation of RC Transient)

By Laplace Transform

$$V = Ri(t) + \frac{1}{C} \int_0^t i(t) dt + V'$$

$$V_s = RI(s) + \frac{I(s)}{Cs} + \frac{V'}{s} \rightarrow 0$$

$$I(s) = \frac{V_s}{R + \frac{1}{Cs}}$$

$$i(t) = \frac{V}{R} e^{-t/RC}$$

① With DC a/p

$$i(t) = \frac{V}{R} e^{-t/\tau}$$

② With unit step

$$i(t) = \frac{1}{R} e^{-t/\tau}$$

③ Impulse response

$$= \frac{d}{dt} [\text{unit step response}]$$

$$\frac{d}{dt} [V(t)] = \frac{d}{dt} [1 \delta t]$$

$$= \frac{d}{dt} \left[\frac{1}{R} e^{-t/\tau} \right]$$

$$= -\frac{1}{R\tau} e^{-t/\tau}$$

④ Ramp response


$$= \int_0^t \frac{1}{R} e^{-t/\tau} dt$$

$$\int u(t) dt = t$$

⑤ Exponential response

$$e^{-t} = Ri(t) + \frac{1}{C} \int_0^t i(t) dt$$
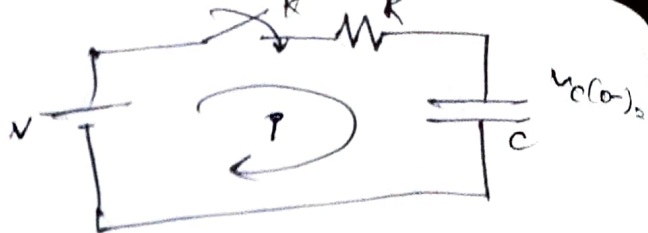
$$-e^{-t} = R \frac{di}{dt} + \frac{i}{C}$$



$$\frac{1}{C} \int_0^t i(t) dt = \frac{1}{C} \int_{-\infty}^0 i(t) dt + \frac{1}{C} \int_0^t i(t) dt$$

$$u(t) \rightarrow \frac{1}{s}$$

$$\delta(t) \rightarrow 1$$

$$t \rightarrow \frac{1}{s^2}$$

$$e^{-at} \rightarrow \frac{1}{s+a}$$

$$A \sin \omega t \rightarrow \frac{A\omega}{s^2 + \omega^2}$$

$$A \cos \omega t \rightarrow \frac{As}{s^2 + \omega^2}$$

$$\frac{df}{dt} \rightarrow sF(s) - f(0)$$


$$\int_0^t f(t) dt \rightarrow \frac{F(s)}{s}$$

$$\int_{-\infty}^t f(t) dt \rightarrow \frac{F(s)}{s} + \frac{f(0)}{s}$$

$$\left(D + \frac{1}{RC}\right) i = -\frac{e^{-t}}{R}$$

First Order Non-homogeneous D.E

RC Transient

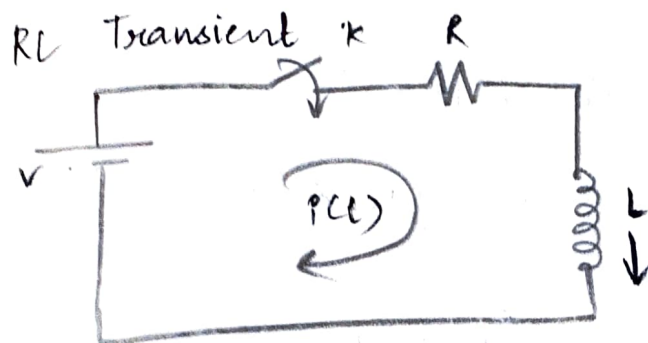

Find $i(t)$ for $t > 0$

$$V = Ri(t) + L \frac{di}{dt}$$

$$i_L(0) = 0$$

$$\left(D + \frac{R}{L}\right) i = \frac{V}{L}$$

1st order H.D.E

$$\tau = \frac{L}{R}$$

$$i(t) = i_c(t) + i_p(t)$$

complementary particular

$$i(t) = k e^{-t/\tau} \rightarrow \text{complementary}$$

$$+ e^{t/\tau} \int e^{-t/\tau} \cdot \frac{V}{L} dt$$

$$i(t) = k e^{-t/\tau} + e^{-t/\tau} \int e^{t/\tau} \cdot \frac{V}{L} dt = k e^{-t/\tau} + \frac{V}{R}$$

Initially
 $L \rightarrow$ open

$$i(0+) = 0 = k \times 1 + \frac{V}{R}$$

$$V = -\frac{V}{R}$$

$$i(t) = \frac{V}{R} [1 - e^{-t/\tau}]$$


On steady state

$L \rightarrow$ short circuit

$$i(t) = \frac{V}{R} (1 - e^{-t/\tau}) \quad | \quad i(\infty) = \frac{V}{R}$$

$$V_R(t) = V(1 - e^{-t/\tau})$$
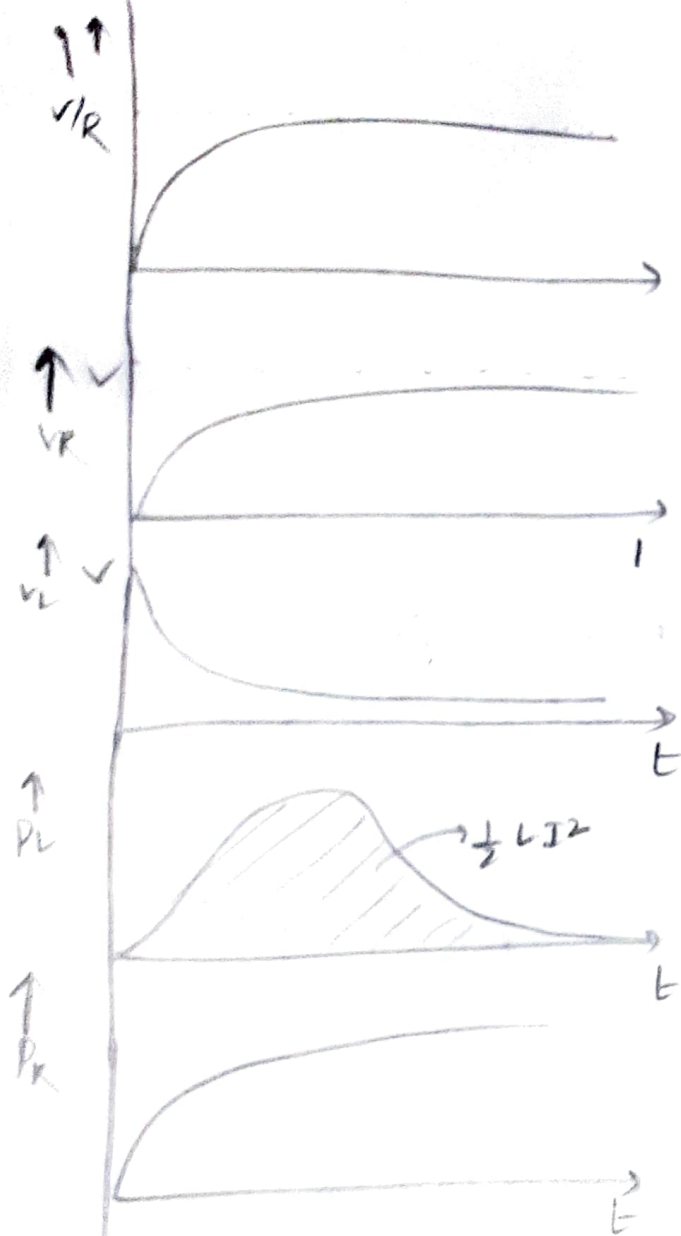
$$V_L(t) = L \frac{di}{dt} = V e^{-t/\tau}$$



$$P_L(t) = V e^{-t/\tau} \frac{V}{R} (1 - e^{-t/\tau})$$

$$= \frac{V^2}{R} (e^{-t/\tau} - e^{-2t/\tau})$$

$$E_L = \int_0^{\infty} P_L(t) dt = \frac{1}{2} L \left(\frac{V}{R} \right)^2$$

$$V = R i(t) + L \frac{di}{dt}$$

$$P_R = V(1 - e^{-t/\tau}) \frac{V}{R} (1 - e^{-t/\tau})$$

$$= \frac{V^2}{R} (1 - e^{-t/\tau})^2$$

$$E_R = \int_0^{\infty} P_R(t) dt = \infty$$

$$\eta = \frac{\frac{1}{2} L I^2}{\infty} \equiv 0\%$$

22nd August 2019

Second order RLC Series.

Find $i(t)$ for $t > 0$


$$V = R i(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) dt$$

$$0 = R \frac{di}{dt} + L \frac{d^2 i}{dt^2} + \frac{1}{C} i$$

$$\left(D^2 + \frac{R}{L} D + \frac{1}{LC} \right) i = 0$$

Second order homogeneous D.E

Complete H.W.S

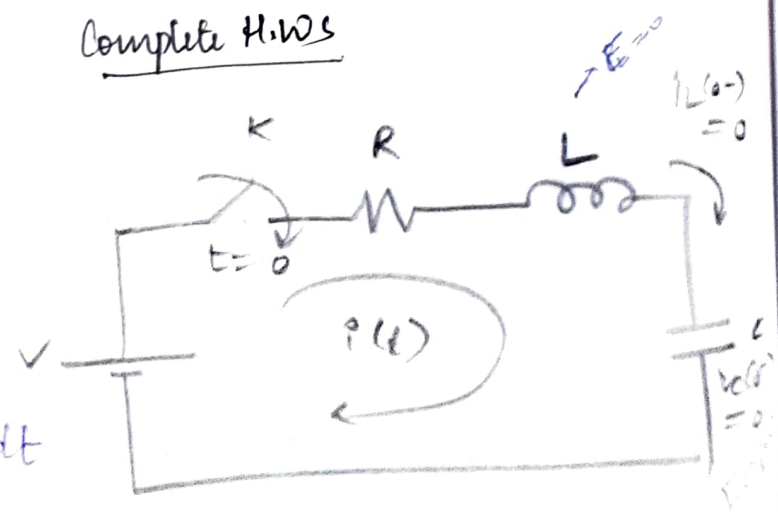

$i(t) = i_c(t)$
depends on nature of roots.

$$r_{1,2} = \frac{-\frac{R}{L} \pm \sqrt{\left(\frac{R}{L}\right)^2 - 4 \times \frac{1}{LC}}}{2 \times 1}$$

$$r_{1,2} = \frac{-R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$\text{Let } \alpha = \frac{-R}{2L}; \beta = \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}$$

$$r_1 = \alpha + \beta$$

$$r_2 = \alpha - \beta$$

Case 1: If $\left(\frac{R}{2L}\right)^2 > \frac{1}{LC}$, two roots are real and not equal.
overdamping

$$i(t) = k_1 e^{(\alpha+\beta)t} + k_2 e^{(\alpha-\beta)t}$$

$k_1, k_2 \rightarrow \text{constant}$

Case 2: If $\left(\frac{R}{2L}\right)^2 = \frac{1}{LC}$ ($\beta=0$)

$r_1 = \alpha, r_2 = \alpha$, Two roots are ~~eq~~ real and equal.
critically damped

$$i(t) = e^{\alpha t} (k_1 + k_2 t)$$

Case 3: If $\left(\frac{R}{2L}\right)^2 < \frac{1}{LC}$ two roots are complex and conjugate of each other
underdamped

$$i(t) = e^{\alpha t} [k_1 \cos \beta t + k_2 \sin \beta t]$$

I) $i(0+) = 0$

II) $V = Ri(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) dt$; at $t=0+$

$$V = R i(0+) + L \frac{di(0+)}{dt} + \frac{1}{C} \int_0^{0+} i(t) dt$$

$$V = 0 + L \frac{di(0+)}{dt} + 0$$

$$\therefore \frac{di(0+)}{dt} = \frac{V}{L}$$

① $0 = k_1 + k_2 \rightarrow$ ①

Differentiale

$$i(t) = k_1 e^{(\alpha+\beta)t} + k_2 e^{(\alpha-\beta)t}$$

$$\frac{di(t)}{dt} = k_1(\alpha+\beta) e^{(\alpha+\beta)t} + k_2(\alpha-\beta) e^{(\alpha-\beta)t}$$

at $t=0$ $\frac{V}{L} = k_1(\alpha+\beta) + k_2(\alpha-\beta)$

$$\frac{V}{L} = \alpha(k_1 + k_2) + \beta(k_1 - k_2)$$

$$\frac{V}{L} = \beta(k_1 - k_2)$$

$$k_1 - k_2 = \frac{V}{\beta L}$$

$$k_1 + k_2 = 0$$

$$2k_1 = \frac{V}{\beta L} \Rightarrow k_1 = \frac{V}{2\beta L}$$

$$k_1 = \frac{V}{2\beta L}, k_2 = -\frac{V}{2\beta L}$$

$$k_2 = \frac{V}{2\beta L} - \frac{V}{\beta L} = -\frac{V}{2\beta L}$$

H.W

②

$$i(t) = e^{\alpha t}(k_1 + k_2 t)$$

$$0 = k_1$$

Diff $i(t) = e^{\alpha t}(k_1 + k_2 t)$

$$\frac{di(t)}{dt} = e^{\alpha t}(k_2) + \alpha(k_1 + k_2 t) e^{\alpha t}$$

at $t=0$

$$\frac{V}{L} = k_2 + \alpha k_1$$

$$k_2 = \frac{V}{L}$$

$$k_1 = 0$$

$$(3). i(t) = e^{\alpha t} [k_1 \cos \beta t + k_2 \sin \beta t]$$

$$\boxed{0 = k_1}$$

$$i(t) = e^{\alpha t} [-k_1 \beta \sin \beta t + k_2 \cos \beta t] + [k_1 \cos \beta t + k_2 \sin \beta t] \alpha e^{\alpha t}$$

at $t=0$

$$\frac{V}{L} = [0 + k_2] + [k_1] \alpha$$

$$k_2 = \frac{V}{L}$$

Apply Laplace Transform

$$V = R i(t) + L \frac{di}{dt} + \frac{1}{C} \int_0^t i(t) dt$$

$$\frac{V}{s} = R I(s) + L [s I(s) - I(0^-)] + \frac{I(s)}{Cs}$$


$$I(s) [R + Ls + \frac{1}{Cs}] = \frac{V}{s}$$

$$I(s) \left[\frac{CRs + CLs^2 + 1}{C} \right] = V$$

$$I(s) = \frac{VC}{1 + CRs + CLs^2} = \frac{VC}{CLs^2 + CRs + 1} = \frac{VC}{s^2 \left(LC + \frac{CR}{s} + \frac{1}{s^2} \right)}$$


$$I(s) = \frac{VC}{LC \left(s^2 + \frac{RS}{L} + \frac{1}{LC} \right)} = \frac{VC}{LC \left(s^2 + \left(\frac{R}{L} \right) s + \frac{1}{LC} \right)} = \frac{V/L}{\left(s^2 + \left(\frac{R}{L} \right) s + \frac{1}{LC} \right)}$$

Dual of this H.W.

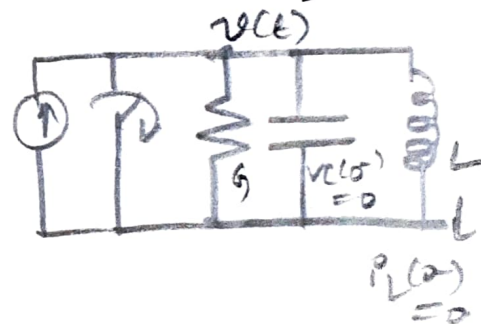

23rd August 2019

AC TRANSIENT:-

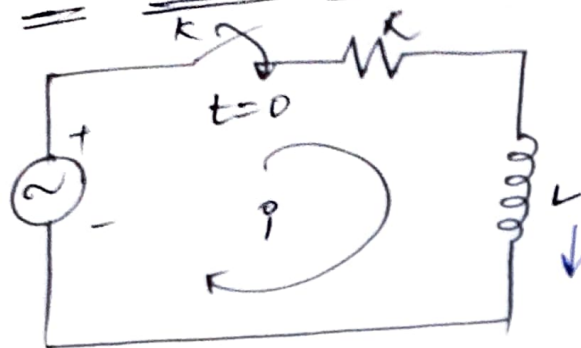

$V = V_m \sin \omega t$
Find $i(t)$ for $t > 0$
(6 combinations)
 $V = V_m \cos(\omega t \pm \phi)$

$$V_m \sin \omega t = R i(t) + L \frac{di}{dt}$$

$$(D + \frac{R}{L}) i = \frac{V_m}{L} \sin \omega t$$

$$i(t) = i_c(t) + i_p(t) = K e^{-t/\tau}$$

Let $i_p = A \sin \omega t + B \cos \omega t$

$$V_m \sin \omega t = R [A \sin \omega t + B \cos \omega t] + L [A \omega \cos \omega t - B \omega \sin \omega t]$$

$$V_m = AR - B\omega L \rightarrow \textcircled{1} \times R$$

$$0 = RB + A\omega L \rightarrow \textcircled{2} \times \omega L$$

Solve for $A =$
 $B =$

$$RV_m = AR^2 - B\omega L$$

$$0 = B\omega L + A\omega^2 L^2$$

$$RV_m = A(R^2 + \omega^2 L^2)$$

$$A = \frac{RV_m}{R^2 + \omega^2 L^2}$$

$$V_m \omega L = -AR\omega L - B\omega^2 L^2$$

$$0 = -R^2 B + AR\omega L$$

$$V_m \omega L = -B(R^2 + \omega^2 L^2)$$

$$B = \frac{-\omega L V_m}{R^2 + \omega^2 L^2}$$

$$\Rightarrow i_p = A \sin \omega t + B \cos \omega t = p \sin(\omega t + b)$$

$$i_p = p [\sin \omega t \cos b + \cos \omega t \sin b]$$

Here $p \cos b = A$; $p \sin b = B$.

$$P = \sqrt{A^2 + B^2} = \frac{(R^2 + \omega^2 L^2) V_m}{(R^2 + \omega^2 L^2)} \quad \left[P = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \right]$$

$$b = \tan^{-1}\left(\frac{B}{A}\right) \Rightarrow \boxed{b = \tan^{-1}\left(\frac{2\omega L}{R}\right)}$$

$$\Rightarrow i(t) = Ke^{-t/\tau} + \frac{V_m \sin(\omega t - \tan^{-1}(\frac{\omega L}{R}))}{\sqrt{R^2 + \omega^2 L^2}}$$

$$i(0^-) = 0 = KX1 + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(-\tan^{-1}(\frac{\omega L}{R}))$$

$$K = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\tan^{-1}(\frac{\omega L}{R}))$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\tan^{-1}(\frac{\omega L}{R})) e^{-t/\tau} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \sin(\omega t - \tan^{-1}(\frac{\omega L}{R}))$$

$i(t)$ using Laplace transforms.

$$V_m \sin \omega t = R i(t) + L \frac{di}{dt}$$

Laplace Transforms

$$\frac{V_m \omega}{\omega^2 + s^2} = R I(s) + L s I(s)$$

$$I(s) = \frac{V_m \cdot \omega}{(s^2 + \omega^2 L^2)(R + Ls)} =$$

$$I(s) = \frac{A}{(Ls + R)} + \frac{Bs + C}{(s^2 + \omega^2 L^2)} = \frac{V_m \omega}{(s^2 + \omega^2 L^2)(R + Ls)}$$

$$A(s^2 + \omega^2 L^2) + (Ls + R)(Bs + C) = V_m \cdot \omega$$

$$s^2(A + BL) + s(CL + BR) + (A\omega^2 + RC) = V_m \cdot \omega$$

$$A + BL = 0$$

$$B = -\frac{A}{L}$$

$$-\frac{A}{L} = -\frac{CL}{R}$$

$$AR = CL^2$$

$$\boxed{A = \frac{CL^2}{R}}$$

$$CL + BR = 0$$

$$B = -\frac{CL}{R}$$

$$A = \frac{CL}{R}$$

$$A\omega^2 + RC = V_m \omega$$

$$A = \frac{CL^2}{R}, \quad C = \frac{AR}{CL}$$

$$B = -\frac{CL}{R}$$

$$\frac{CL^2\omega^2 + RC}{R} = V_m\omega$$

$$C = \frac{V_m \cdot \omega R}{R^2 + \omega^2 L^2}$$

$$A = \frac{V_m \cdot \omega R}{(R^2 + \omega^2 L^2)} \cdot \frac{L^2}{R} = \frac{V_m \omega L^2}{R^2 + \omega^2 L^2}$$

$$A = \frac{V_m \omega L^2}{R^2 + \omega^2 L^2}$$

$$B = \left(\frac{-V_m \omega R}{R^2 + \omega^2 L^2} \right) \frac{L}{R}$$

$$B = \frac{-V_m \omega L}{R^2 + \omega^2 L^2}$$

$$I(s) = \frac{V_m \omega L^2}{(R^2 + \omega^2 L^2)(s + R/L)} + \frac{\left(\frac{-V_m \omega L}{R^2 + \omega^2 L^2} \right) s + \left(\frac{V_m \omega R}{R^2 + \omega^2 L^2} \right)}{s + R/L}$$

Inverse Laplace transform

$$i(t) = \frac{V_m \omega L^2}{(R^2 + \omega^2 L^2)} \cdot \frac{1}{L} e^{-\frac{R}{L}t} + \left[\frac{-V_m \omega L}{R^2 + \omega^2 L^2} \right] \frac{s}{s + R/L} + \frac{V_m \omega R}{R^2 + \omega^2 L^2} \times \frac{1}{s + R/L}$$

$$i(t) = \frac{V_m \omega L}{R^2 + \omega^2 L^2} e^{-\frac{R}{L}t} - \frac{V_m \omega L}{R^2 + \omega^2 L^2} \cos \omega t + \frac{V_m R}{(R^2 + \omega^2 L^2)} \sin \omega t$$

$$i(t) = \frac{V_m \omega L e^{-\frac{R}{L}t}}{(R^2 + \omega^2 L^2)} - \frac{V_m \omega L}{(R^2 + \omega^2 L^2)} \cos \omega t + \frac{V_m R \sin \omega t}{R^2 + \omega^2 L^2}$$

$$i(t) = \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} (\sin \omega t \cos(\tan^{-1}(\frac{\omega L}{R})) - \cos \omega t \sin(\tan^{-1}(\frac{\omega L}{R})))$$


$$i(t) = \frac{V_m \omega L}{R^2 + \omega^2 L^2} + \frac{V_m}{\sqrt{R^2 + \omega^2 L^2}} \left(\sin \omega t \frac{R}{\sqrt{\omega^2 L^2 + R^2}} \right) - \cos \omega t \left(\frac{\omega L}{\sqrt{R^2 + \omega^2 L^2}} \right)$$

$$i(t) = \frac{V_m \omega L}{R^2 + \omega^2 L^2} + \frac{V_m}{R^2 + \omega^2 L^2} (R \sin \omega t - \omega L \cos \omega t)$$

$$i(t) = \frac{V_m \omega L e^{-Rt/L}}{R^2 + \omega^2 L^2} + \frac{V_m R_2 \cos \omega t}{R^2 + \omega^2 L^2} - \frac{V_m \omega L \cos \omega t}{R^2 + \omega^2 L^2}$$

28th August 2019

* Single pole double throw switch

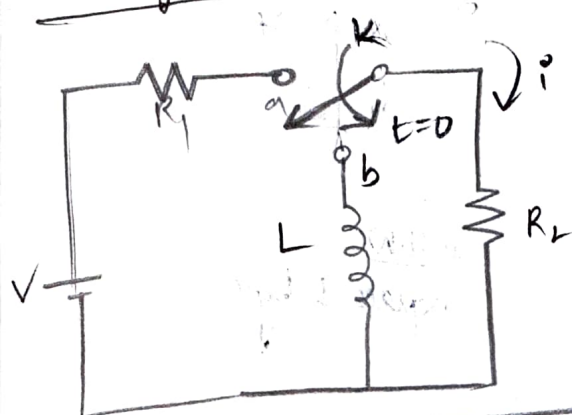


Switch K connected to a, until it reaches steady state and moves to b at $t=0$. Find $i(t)$ for $t > -\infty$.
 $-\infty$ to 0^- a)
 0^+ to $+\infty$ b)

$$V_C(0^+) = V_C(0^-) = V$$

$$i(t) = i_f + (i_i - i_f) e^{-t/\tau}$$

~~valid~~ valid only to 1st order CKE

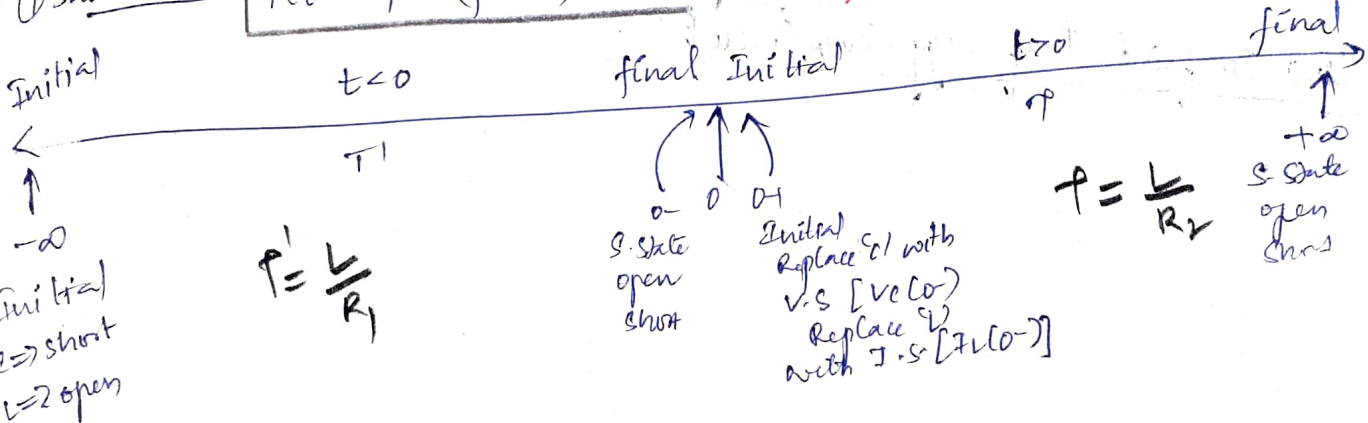
① Short-Cut $i(t) = i_f + (i_i - i_f) e^{-t/\tau'}$



$$\tau' = \frac{L}{R_1}$$

$$\tau = \frac{L}{R_2}$$

at $t=0^-$ (s.s)

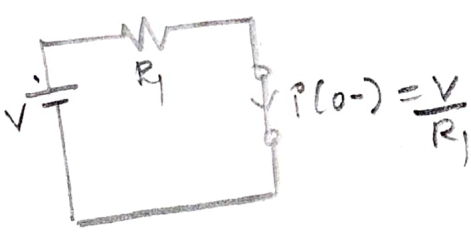

at $t=0^+$
 Since $i(0^+) = \frac{V}{R_1}$
 [Sudden change in current in L not allowed].
 $i(\infty) = 0$.


$$i(t) = 0 + \left(\frac{V}{R_1} - 0\right) e^{-t/\tau}$$

$$i(t) = \frac{V}{R_1} e^{-t/\tau}$$

$$i(t) = i_f + (i_i - i_f) e^{-t/\tau}$$

$$= 0 + \left(\frac{V}{R_1} - 0\right) e^{-t/\tau}$$

$$= \frac{V}{R_1} e^{-t/\tau}$$

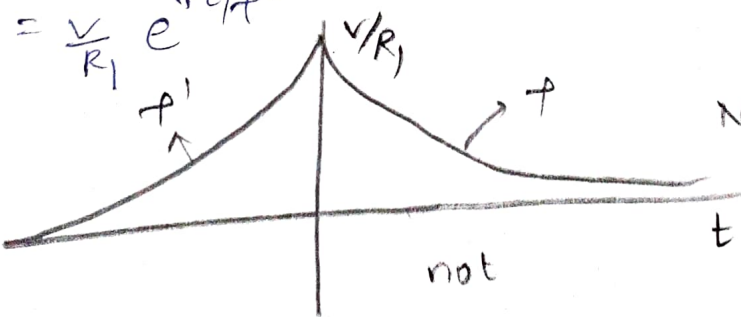

Need not be symmetrical!

Mesh Analysis
 $L \frac{di}{dt} + R_2 i = 0$

② Mathematical Approach
 i

③ Laplace Transform

$(D + \frac{R_2}{L}) i = 0$

$i = K e^{-\frac{t}{\tau}}$ where $\tau = \frac{L}{R_2}$

$i(0+) = i(0-) = \frac{V}{R_1} = K \times 1$



$K = \frac{V}{R_1}$

$i = \frac{V}{R_1} e^{-t/\tau}$

How to find τ of any given circuit? ^{1st order}

★ H.W
 Replace L by ∞

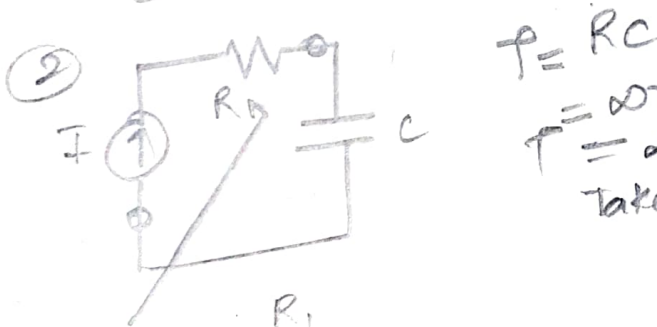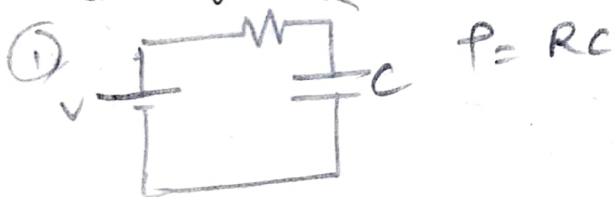★ $\tau = R_T (C_{eq})$ ^{source}
 $V \rightarrow \text{short}$
 $I \rightarrow \text{Open}$



R equivalent looking from C


$\tau = \infty \times C$
 $\tau = \infty$

Is $\tau = \infty$, $t_r = \infty$,
 Takes infinite time to reach steady state




$\tau = (R_1 || R_2) C$

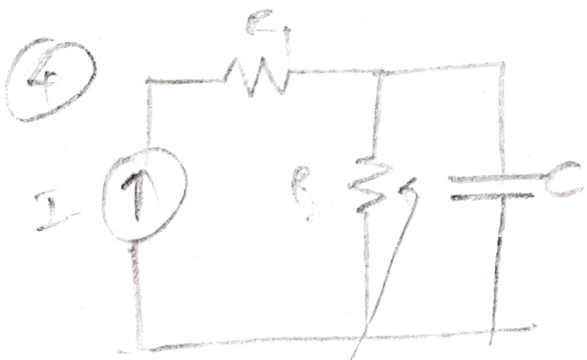
$\tau = \left(\frac{R_1 R_2}{R_1 + R_2} \right) C$



$\tau = R_2 C$

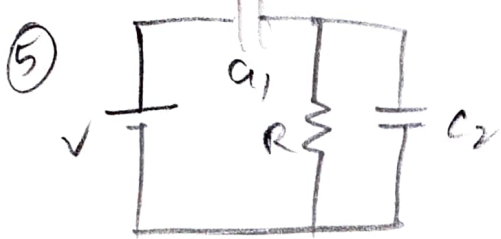


$$\tau = RC_1 + C_2$$

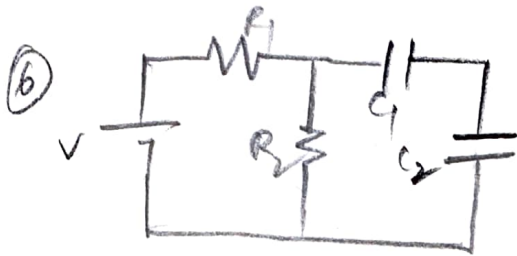


$$\tau = (R_1 \parallel R_2) \frac{C_1 C_2}{C_1 + C_2}$$


* H.W
Replace C by L
Find τ .

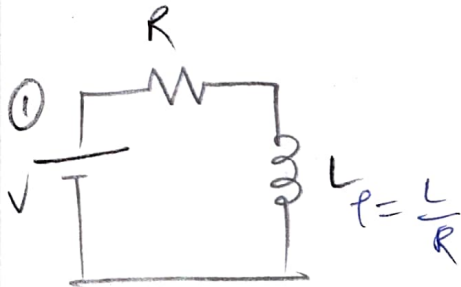


$$\tau = \frac{L}{R}$$

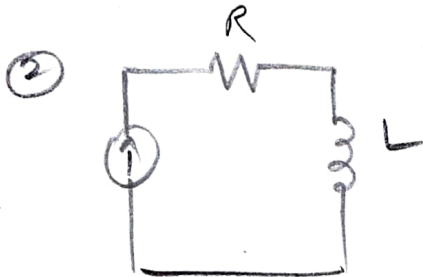

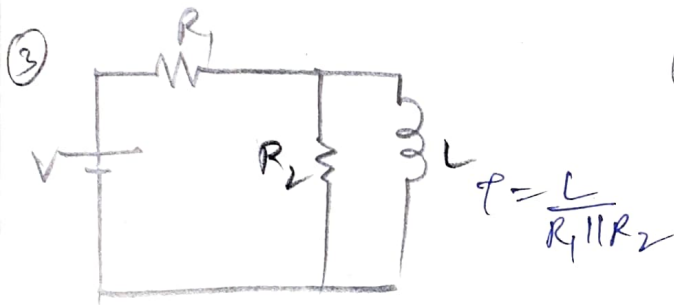
$$\tau = \frac{L}{R} = \frac{L}{\infty} = 0$$




$$\tau = \frac{L}{R_1 \parallel R_2}$$

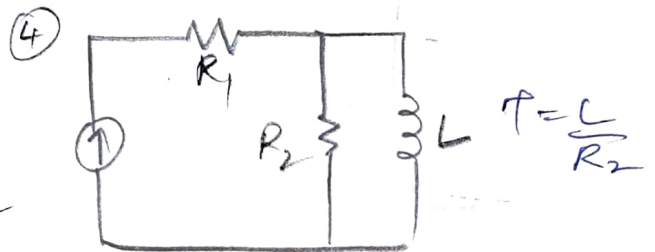

$$\tau = \frac{L}{R_2}$$

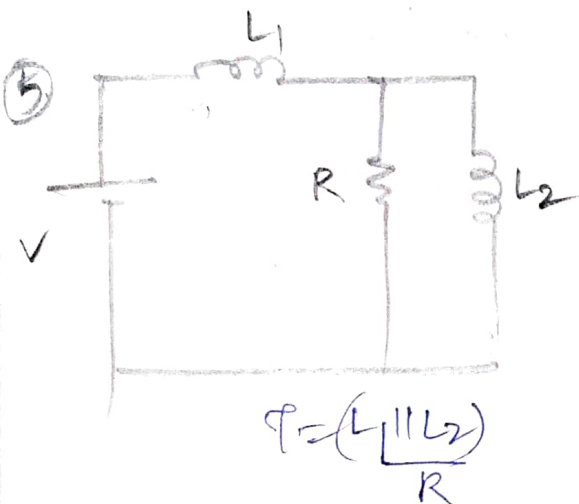

$$\tau = \frac{L_1 \parallel L_2}{R}$$

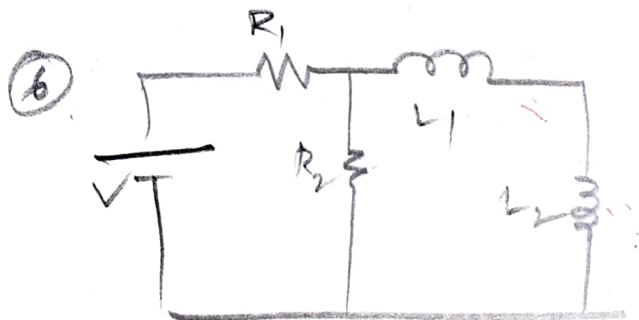

$$\tau = \frac{L_1 + L_2}{R_1 \parallel R_2}$$